

Efficient Time-Domain Simulation and Optimization of Digital FET Circuits


Andrew R. Conn

Ruud A. Haring

Chandu Visweswariah



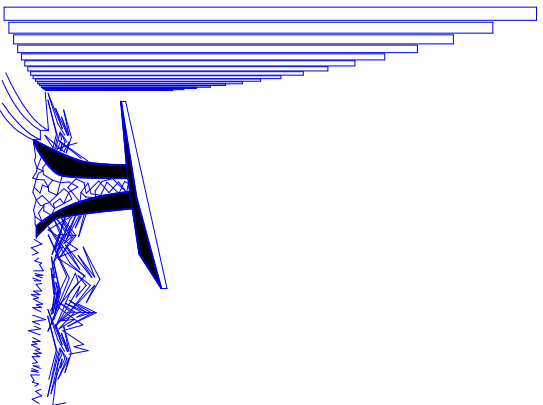**Thomas J. Watson Research Center
Yorktown Heights, NY 10598**




Outline

1. Motivation
2. Circuit analysis (SPECS)
3. Time-domain gradient computation (SPECS)
4. Circuit optimization (JiffyTune with LANCELOT)
5. Conclusions and future work

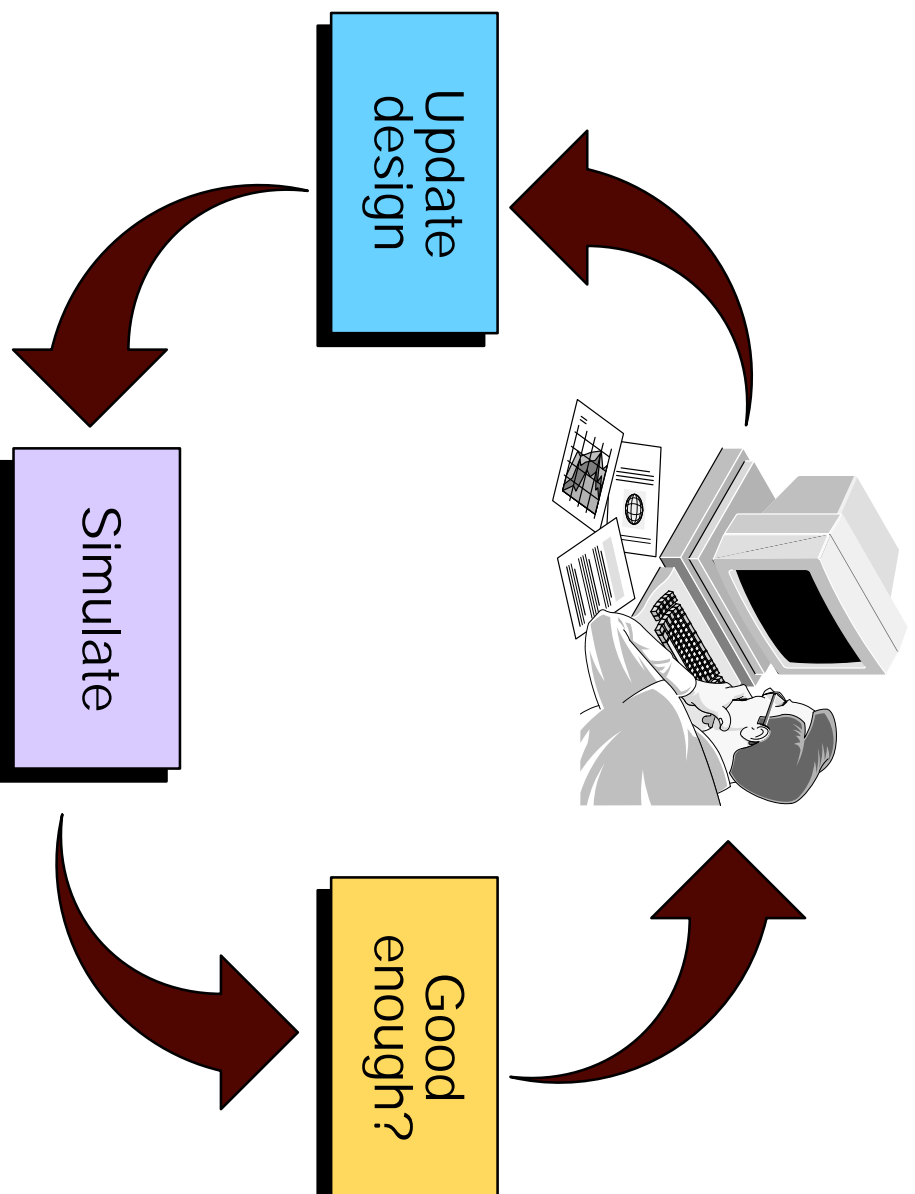
Part 1: Motivation

- *optimization* of custom, high-performance digital circuits is usually a tedious, manual process
- the time spent in closing the loop on delay, area and power requirements is too long



Motivation

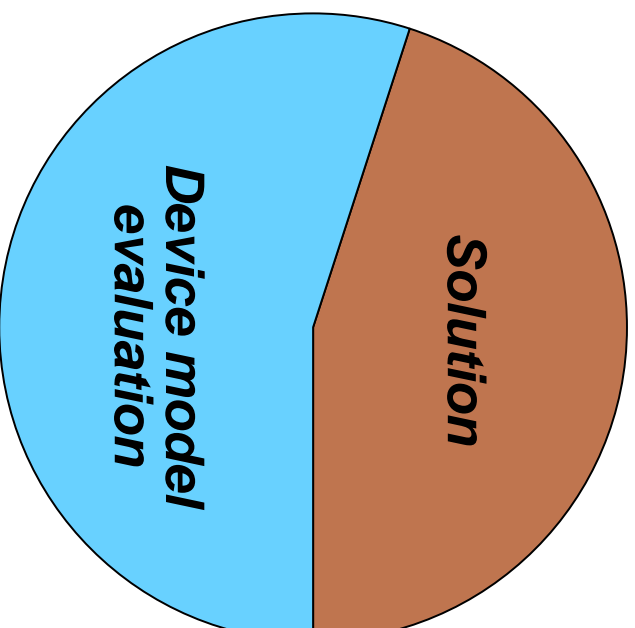
- circuit analysis is computationally expensive
 - evaluation of device modeling equations
 - equation solution



- **must attack both segments!**


Motivation

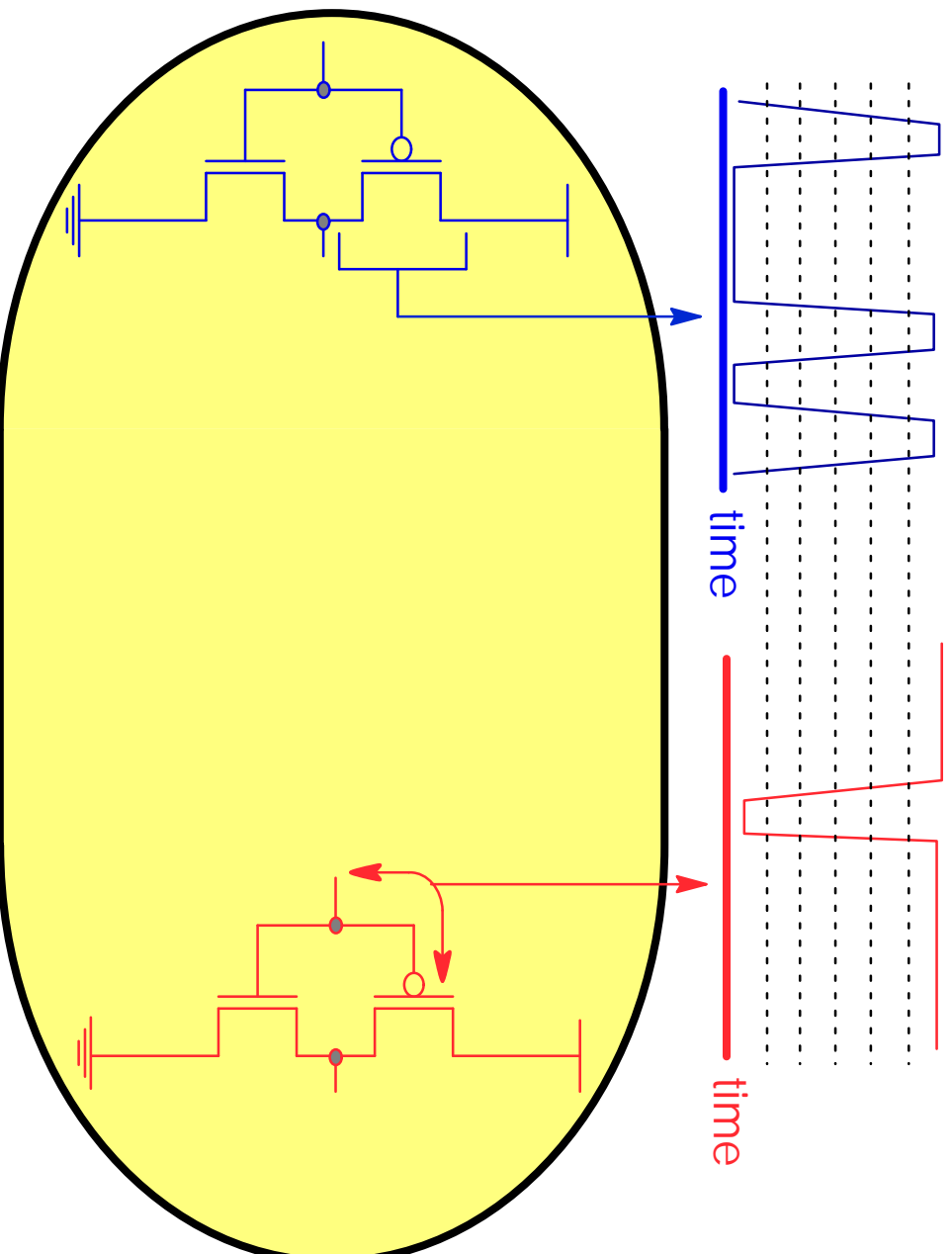- activity factor of a digital circuit is usually low; try to exploit this multi-rate or latency behavior



Motivation

- avoid the accuracy overkill
- variable accuracy analysis is useful for critical path analysis

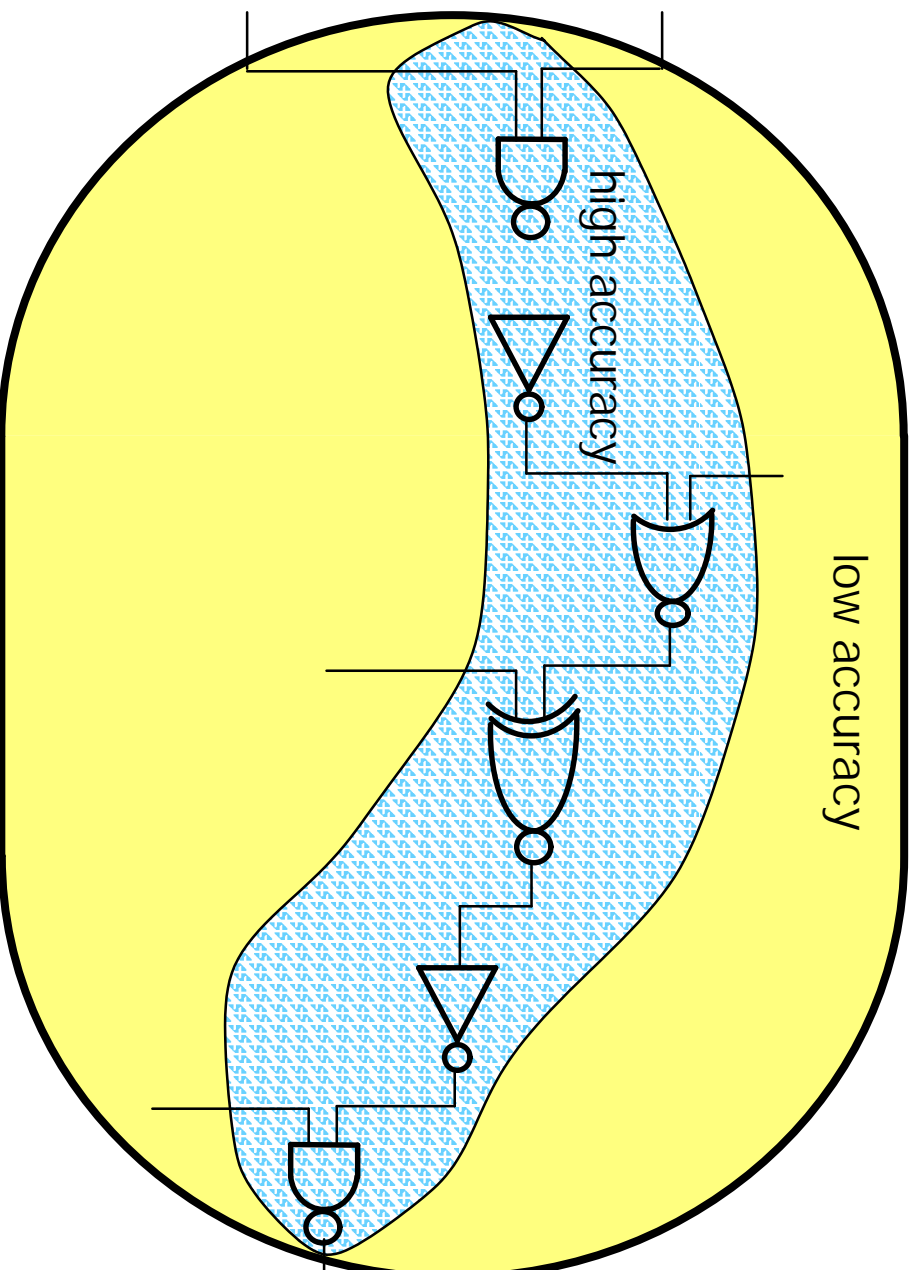

Part 2: Circuit Analysis

Classical circuit analysis

Consider a circuit with nonlinear capacitors (C's), nonlinear resistive elements and current sources (L's).

$$C_C \dot{v}_C + A_L i_L = \mathbf{0}$$

where C_C = capacitance matrix

i_C , v_C = currents, voltages of the C's

i_L , v_L = currents, voltages of the L's

A_L = incidence matrix of the L's

Now model $i_L = Y v_L + J$ (admittance formulation).

$$C_C \dot{v}_C + A_L (Y v_L + J) = \mathbf{0}$$


$$\dot{v}_C = - C_C^{-1} A_L Y v_L - C_C^{-1} A_L J$$

But since $v_L = A_L^T v_C$,

$$\dot{v}_C = - C_C^{-1} A_L Y A_L^T v_C - C_C^{-1} A_L J$$

- of the general form $\dot{x} = \hat{A}x + \hat{B}u$
- coupled, nonlinear DAEs


Classical Circuit Analysis

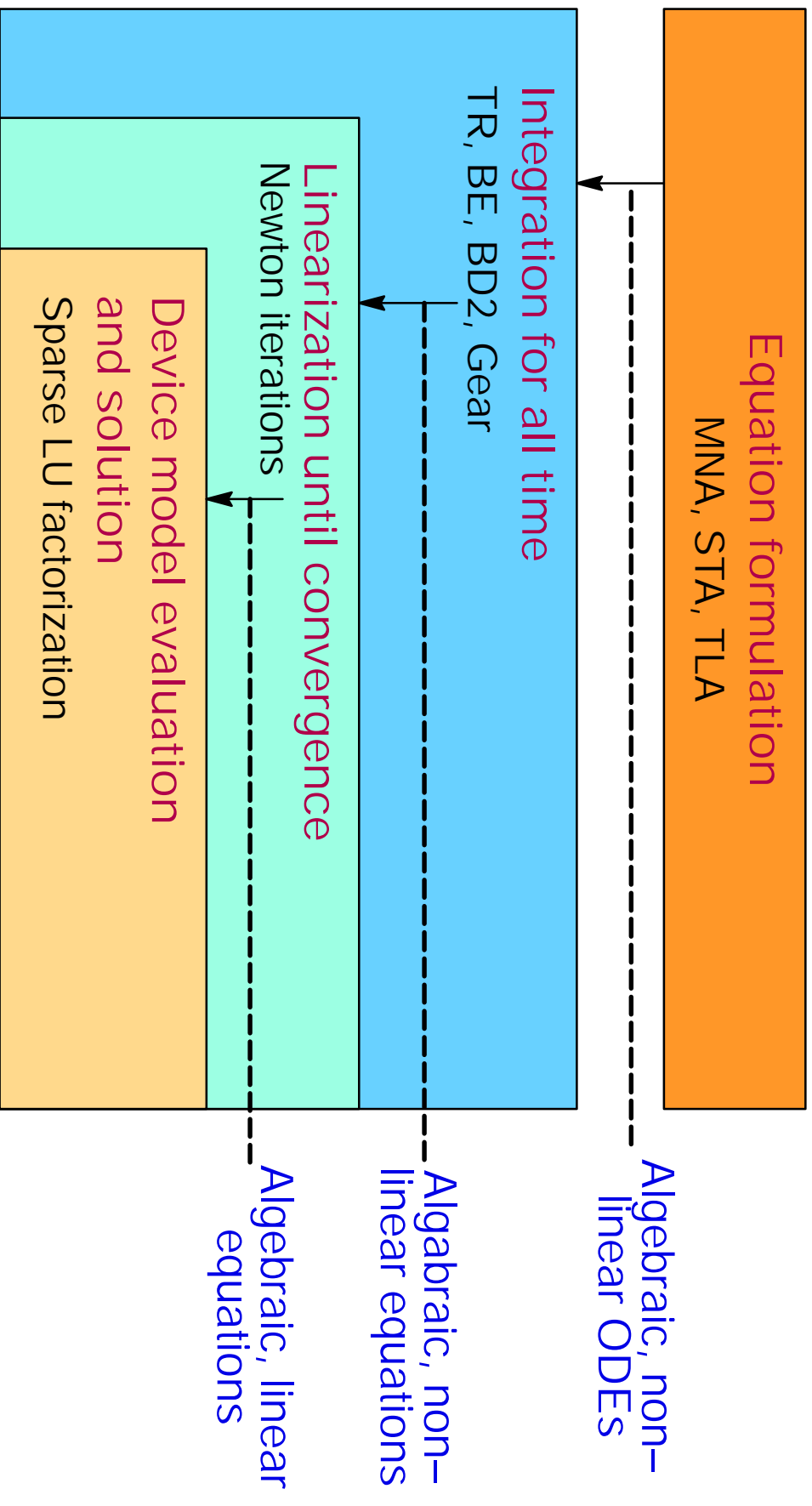

- 1% relative timing accuracy
- $O(n^{1.4})$ growth of run time with circuit size
- size of circuit analyzed is limited to about 10,000 transistors

SPECS: Key Idea

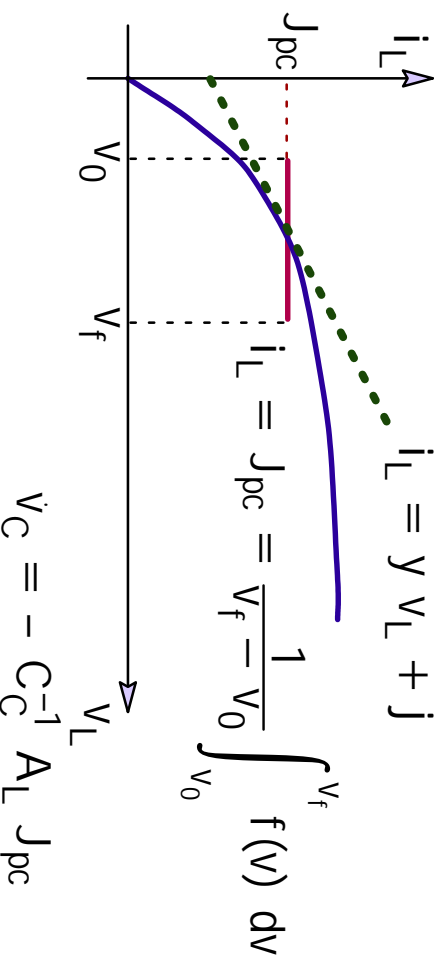
$$\dot{V}_C = -C_C^{-1} A_L Y A_L^T V_C - C_C^{-1} A_L J$$



Implications of this approximation

- nonlinearity of equations eliminated
- if C_C is independent of V_C implicit nature of equations eliminated (i.e., assume that all capacitances are constant)
- if C_C is diagonal, equations are scalar (i.e., all capacitors are grounded)
- all currents are piecewise constant (pwc) in time, voltage slopes are pwc in time, voltages are piecewise linear (pwl) in time
- integration becomes trivial; event-driven analysis possible

SPECS: Modeling and Analysis

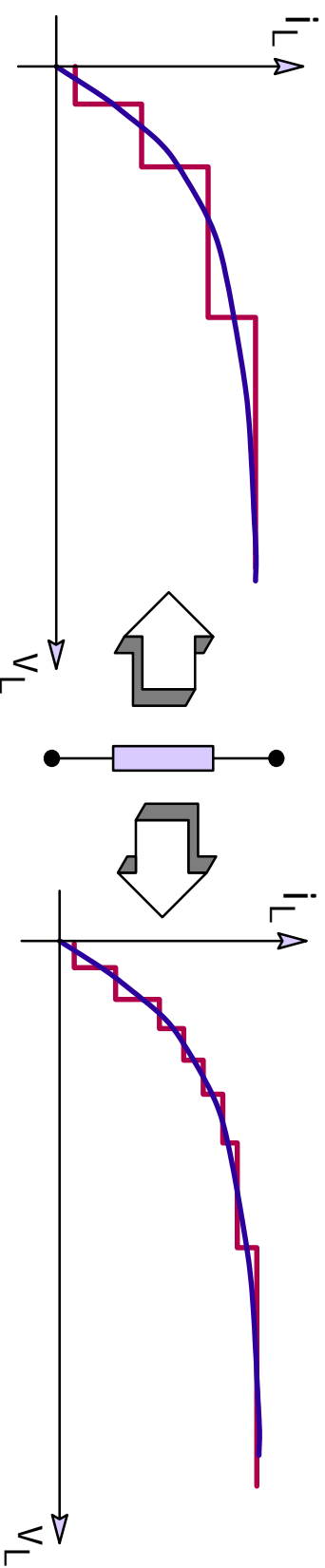

$$\dot{V}_C = -C_C^{-1}A_L J_{pc} \text{ and } \dot{V}_L = -A^T C_C^{-1}A_L J_{pc}$$


1. Every time an element of J_{pc} “jumps,” an event occurs; only one element of i_L changes; update \dot{V}_C and \dot{V}_L .
2. $t_{\text{target}} = \frac{V_{\text{target}} - V_{\text{present}}}{\dot{V}_L}$; update all affected event times.
3. Update the event queue and continue by picking most imminent event on the queue.

- Variable accuracy analysis achieved
- Relative timing error due to approximation is proportional to

$$\left[\frac{\Delta i}{V_L} \right]^2$$



which is very advantageous for digital circuits.

SPECS: The Steady-State Problem

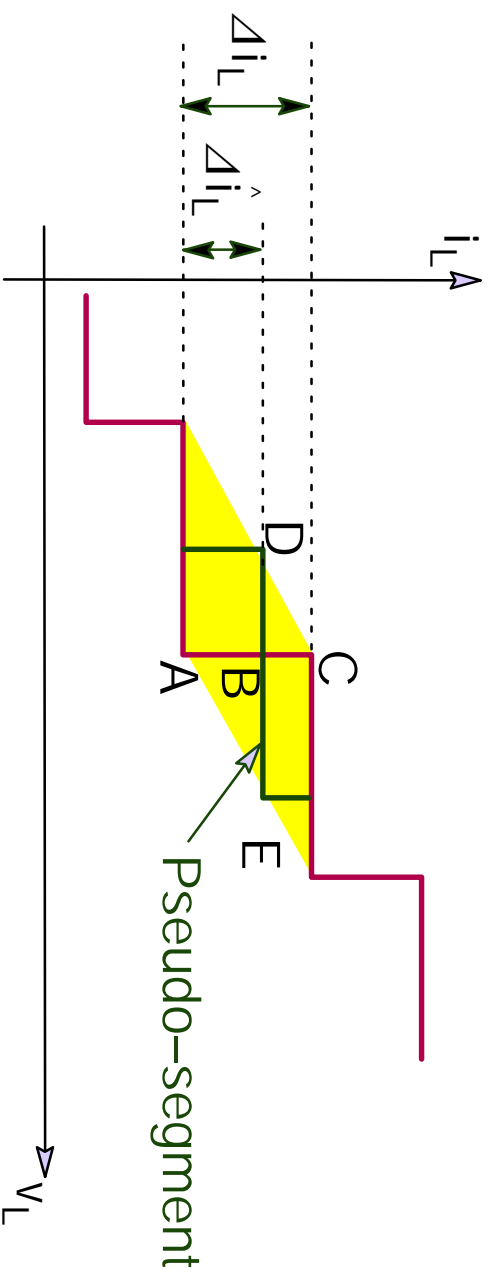

- if $v_L^A > 0$, we have an “increasing event”
- then if $v_L^C = v_L^A - \frac{\Delta i_L}{C_{eq}} < 0$
- find $\Delta \hat{i}_L = v_L^A C_{eq}$ so that $v_L^B = 0$
- interpolate later if necessary to create the pseudo-segment DBE; schedule the element to traverse the segment and reach either D or E
- extend this scheme to multiple dimensions

SPECS: Sample Waveforms

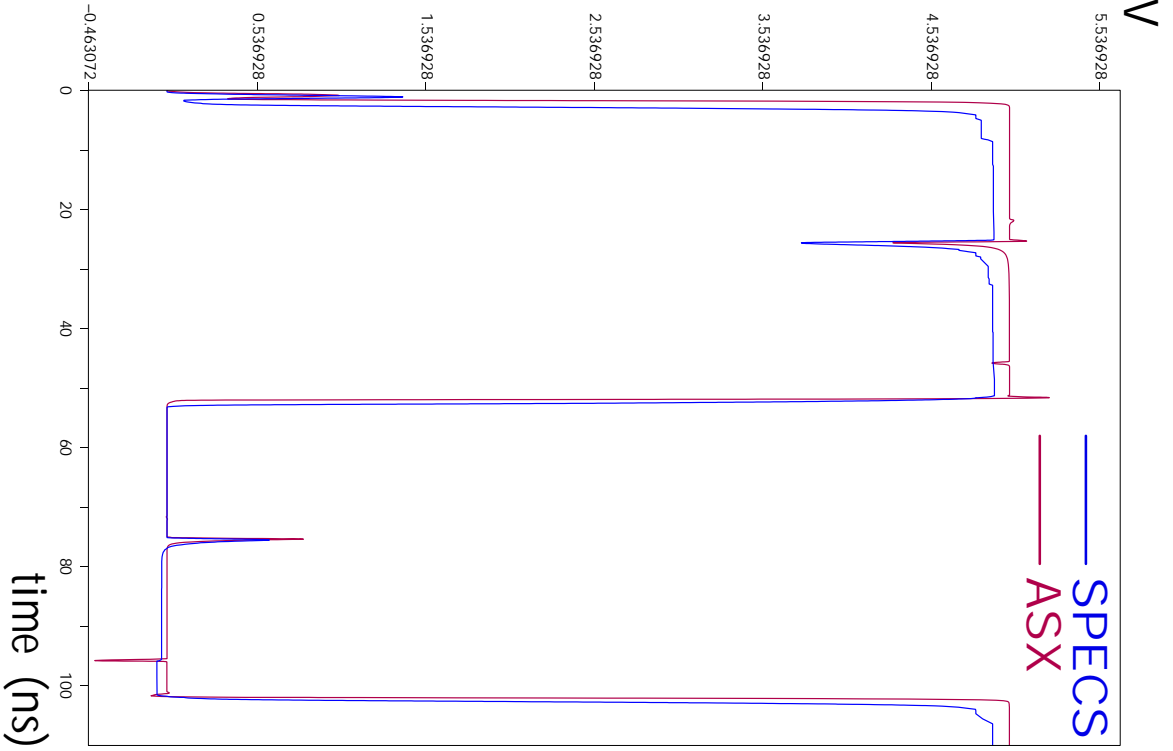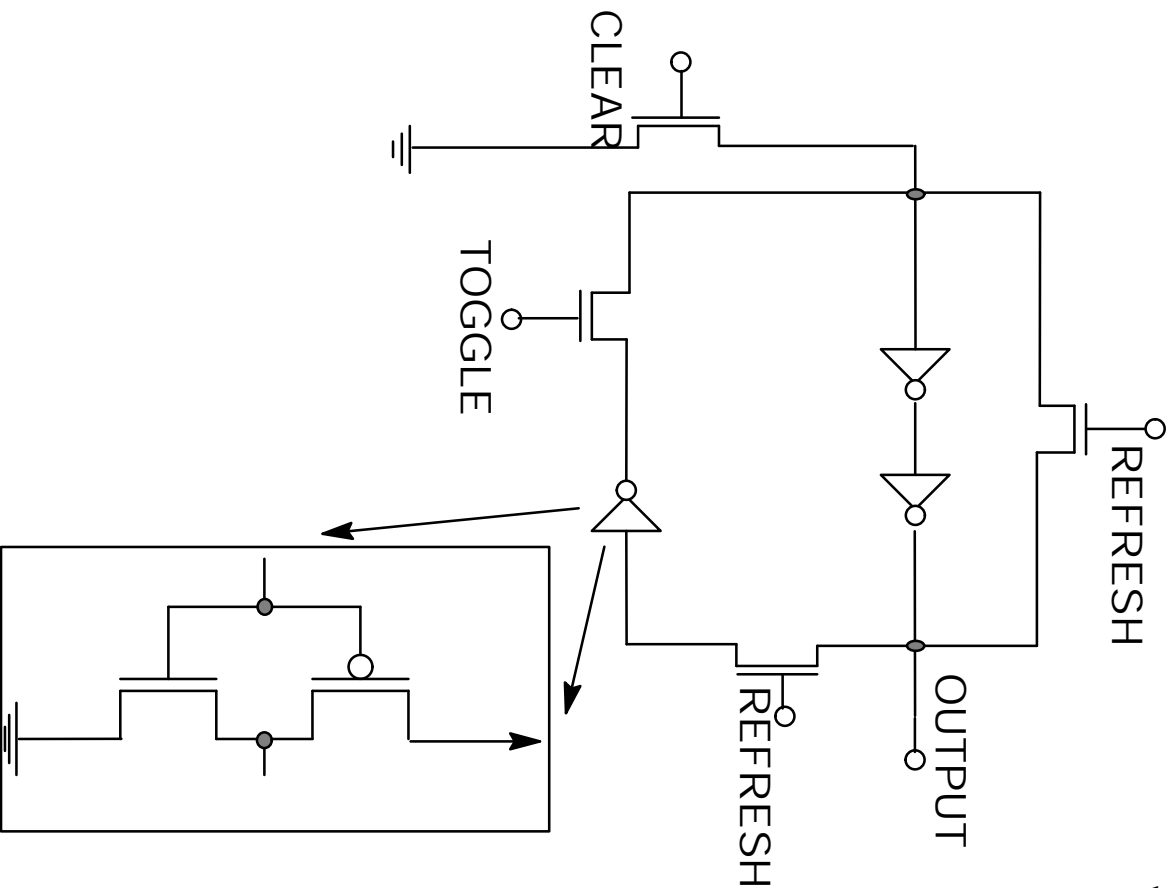

SPECS Summary


Upside

- speed: 70x (6,000 events per second on a workstation)
 - capacity: 10x (0.25M transistors)
 - accuracy: greater than 1σ of delays with 5% relative timing accuracy; worst case is 10%
 - used in 12 IBM sites for
 - timing verification
 - functional verification
 - tuning
 - power estimation
- of digital and memory circuits

Downside

- constant–grounded–capacitance–assumption causes inaccuracy
- stiff circuits a problem
- no inductors
- steady–state level errors incurred

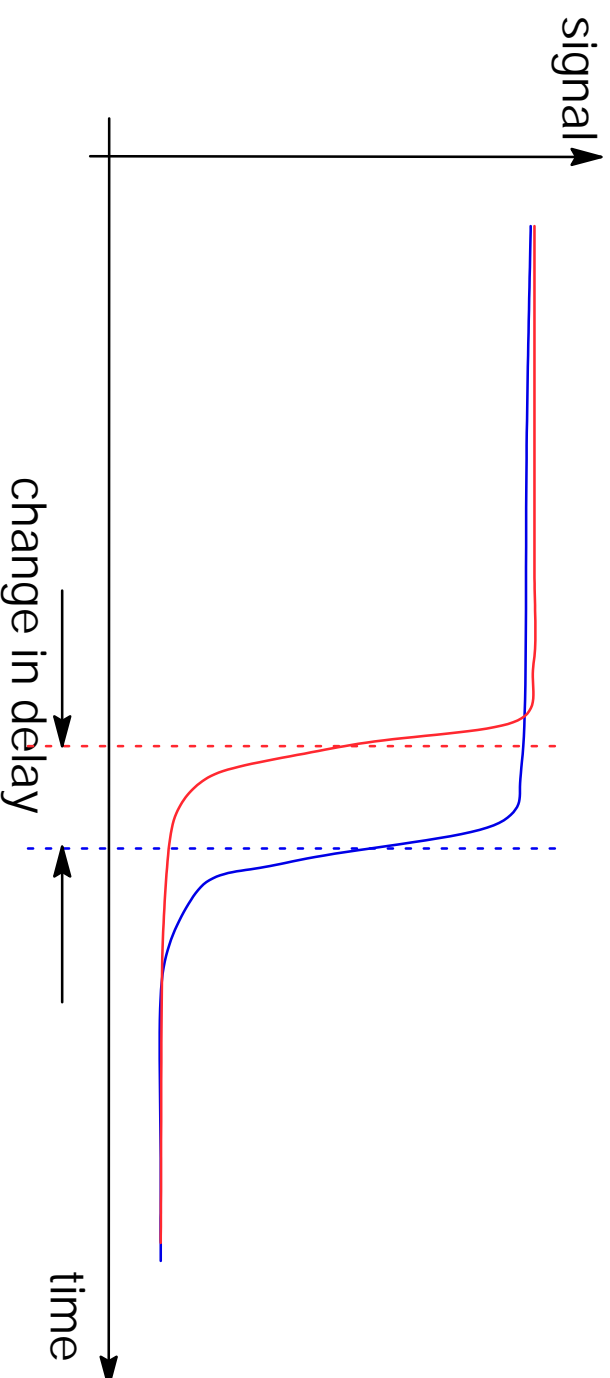
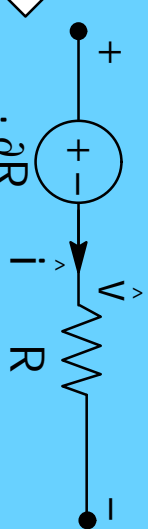

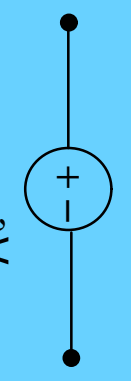
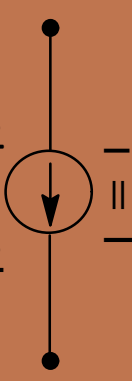
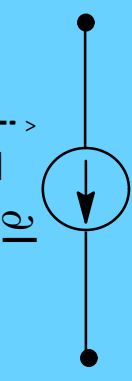

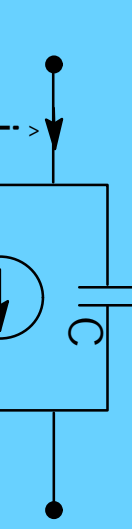
Part 3: Time-Domain Gradients



Sensitivity of delay w.r.t. width = delay/ width

- time-domain sensitivity computation is a unique feature of SPECS
- sensitivity computation is incremental; not by finite difference or perturbation methods
- both the adjoint and direct methods have been implemented
- sensitivity computation is a small overhead on nominal transient simulation run

Sensitivity Analysis by the Direct Method


 $v = iR$ $\frac{\partial v}{\partial p} = i \frac{\partial R}{\partial p} + R \frac{\partial i}{\partial p}$	 $\hat{v} = i \frac{\partial R}{\partial p} + Ri$
 $v = V$ $\frac{\partial v}{\partial p} = \frac{\partial V}{\partial p}$	 $\hat{v} = \frac{\partial v}{\partial p}$
 $i = I$ $\frac{\partial i}{\partial p} = \frac{\partial I}{\partial p}$	 $\hat{i} = \frac{\partial I}{\partial p}$
 $i = C \frac{dv}{dt}$ $\frac{\partial i}{\partial p} = C \frac{\partial}{\partial p} \left(\frac{dv}{dt} \right) + \frac{dv}{dt} \frac{\partial C}{\partial p}$	 $\hat{i} = \frac{\partial C}{\partial p} \frac{dv}{dt} + \frac{\partial C}{\partial p} v$

Key: directly differentiate BCs

Direct Method: Procedure

- replace elements by directly differentiating BCRs to get sensitivity circuit
- reuse LU factors of original solution
- any number of functions, only one parameter

Example:

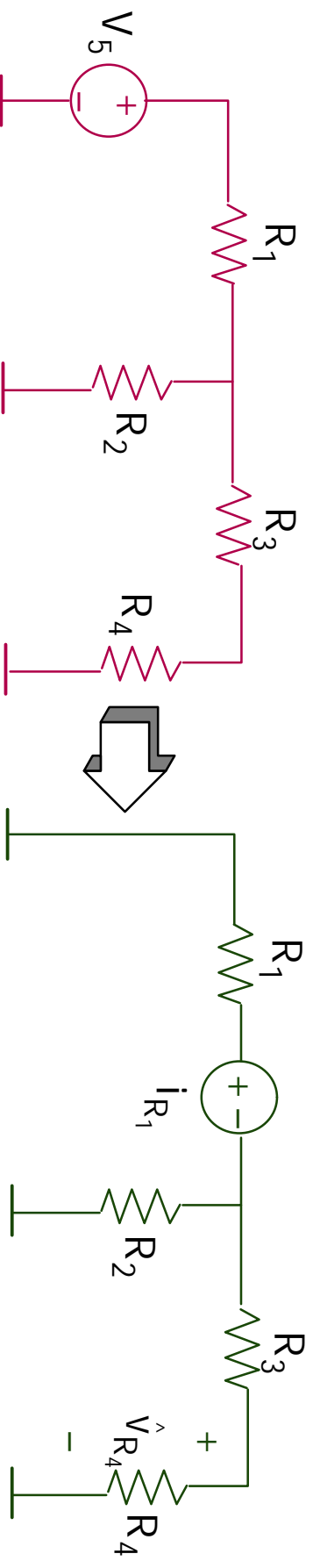

- problem is to find $\frac{\partial V_{R_4}}{\partial R_1}$, so $p = R_1$
- replace V_5 by a short; add a voltage source in series with R_1 ;
solve for \hat{V}_{R_4} ; that is the required answer!

Sensitivity Analysis by the Adjoint Method

Matrix formulation of adjoint method

$$Ax = b$$

$$A \frac{\partial x}{\partial p} + \frac{\partial A}{\partial p} x = \frac{\partial b}{\partial p}$$

Given a scalar function $f(x)$, $\frac{\partial f}{\partial p} = \left[\frac{\partial f}{\partial x} \right]^T \left[\frac{\partial x}{\partial p} \right]$


Postulate $A^T \zeta = \left[\frac{\partial f}{\partial x} \right]$

$$\text{Then } \zeta^T A = \left[\frac{\partial f}{\partial x} \right]^T$$


$$\text{So } \frac{\partial f}{\partial p} = \zeta^T A \left[\frac{\partial x}{\partial p} \right] = \zeta^T \left[\frac{\partial b}{\partial p} - \frac{\partial A}{\partial p} x \right]$$

- re-use LU factors of original solution; LU factors of A^T are U^T and L^T
- any number of parameters, only one function
- electrical formulation based on Tellegen's theorem

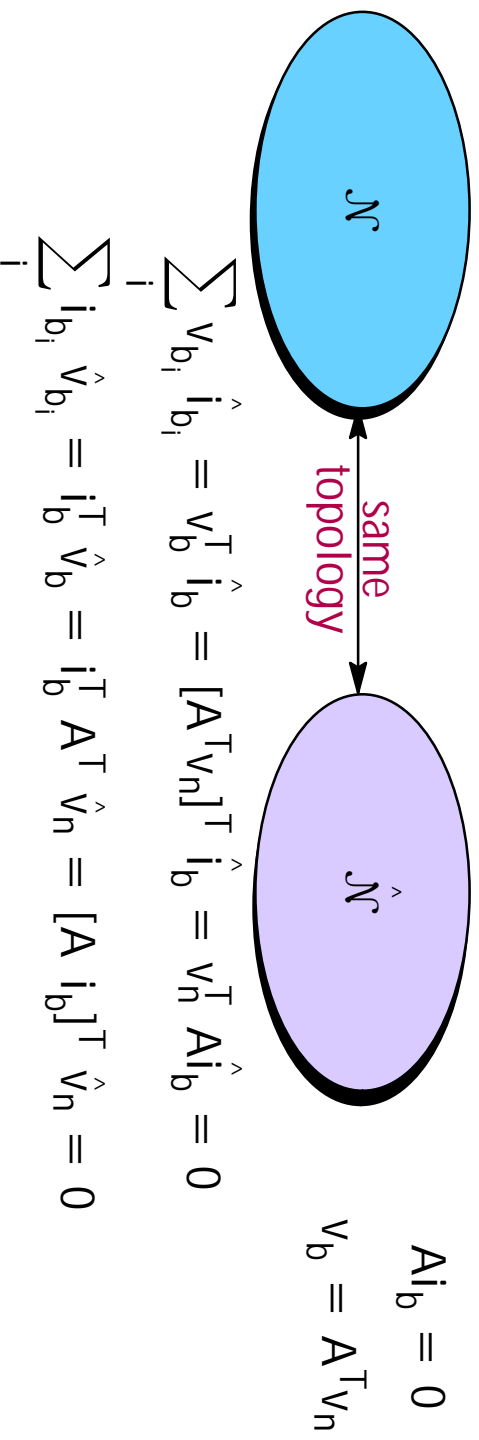Adjoint Sensitivity via Tellegen's Theorem



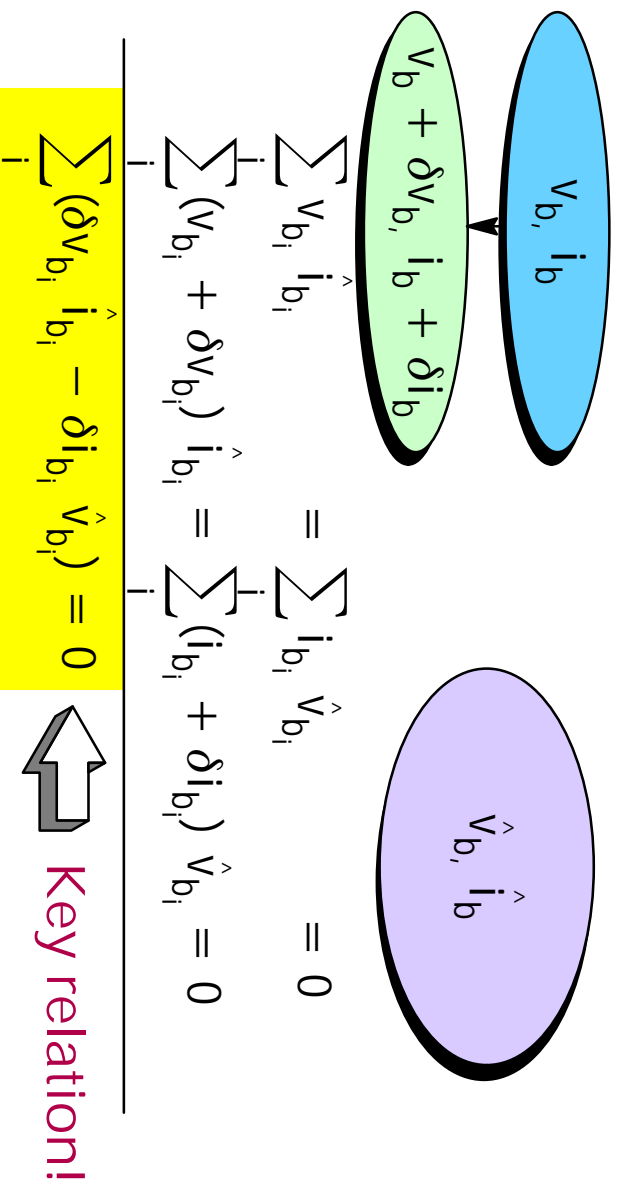Application of Tellegen's theorem to a perturbed circuit



Adjoint Sensitivity Computation

Consider a circuit with only resistors and current sources:

- Current source: $i_j = J_j$; $\delta i_j = \delta J_j$

$$\text{Typical term} = (\delta v_j \hat{i}_j - \delta J_j \hat{v}_j)$$

- Resistor: $v_R = i_R R$; $\delta v_R = i_R \delta R + R \delta i_R + \cancel{\delta R \delta i_R}$

By choosing $\hat{v}_R = R \hat{i}_R$, we get typical term = $i_R \hat{i}_R \delta R$.

- Total circuit: $\sum_{J_s} -\delta v_j \hat{i}_j = \sum_{J_s} -\delta J_j \hat{v}_j + \sum_{R_s} i_R \hat{i}_R \delta R$

- Given a scalar performance function $f(v_j\text{'s})$, $\delta f = \sum \frac{\partial f}{\partial v_j} \delta v_j$.

- Choose $\hat{i}_j = -\frac{\partial f}{\partial v_j}$

- Pick off the required sensitivities:

Thus




$$\frac{\partial f}{\partial J_j} = -\hat{v}_j$$

and

$$\frac{\partial f}{\partial R} = i_R \hat{i}_R$$

- Any number of parameters can be accommodated at once!

Sensitivity Analysis in SPECS

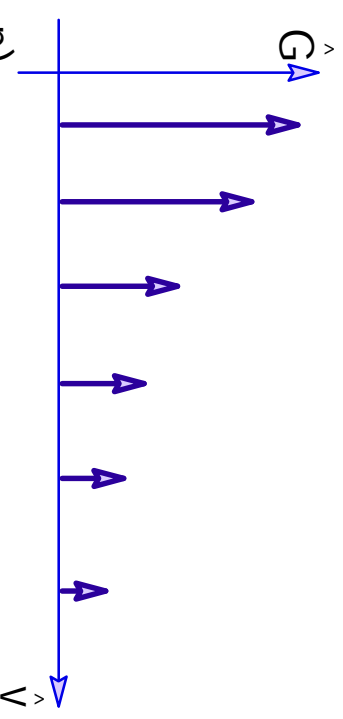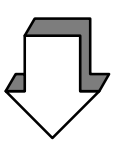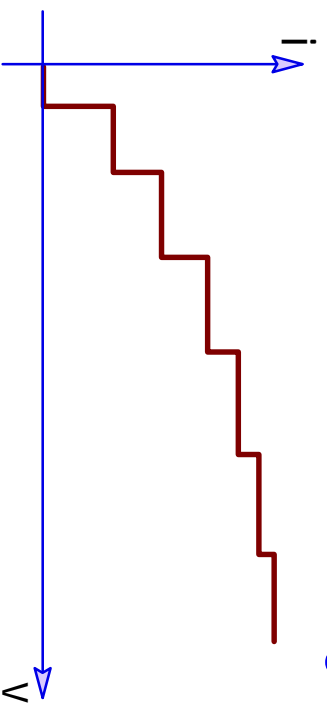

$$i = i(v, p) \quad \text{or} \quad \hat{i} = \hat{G}\hat{v} + \hat{I}_x$$

$$\frac{di}{dp} = \frac{\partial i}{\partial v} \frac{dv}{dp} + \frac{\partial i}{\partial p}$$


- sensitivity or adjoint circuit consists of mostly disconnected capacitors
- little “spurts” of charge sharing occur at the times of the events of the original nominal circuit
- results of sensitivity or adjoint circuit yield required sensitivities; convolution is required in the case of adjoint sensitivity
- compute delay sensitivities as follows:

$$V_{\text{cross}} = V_N \Big|_{t=t_{\text{cross}}}$$

$$\frac{dV_{\text{cross}}}{dt} = 0 = \frac{d}{dp} V_N(t, p) = \frac{\partial V_N}{\partial t} \Big|_{t=t_{\text{cross}}} \frac{dt_{\text{cross}}}{dp} + \frac{\partial V_N}{\partial p} \Big|_{t=t_{\text{cross}}}$$

$$\frac{dt_{\text{cross}}}{dp} = - \frac{\hat{V}_N}{V_N} \Big|_{t=t_{\text{cross}}}$$

Sensitivity Results on Simple Circuit

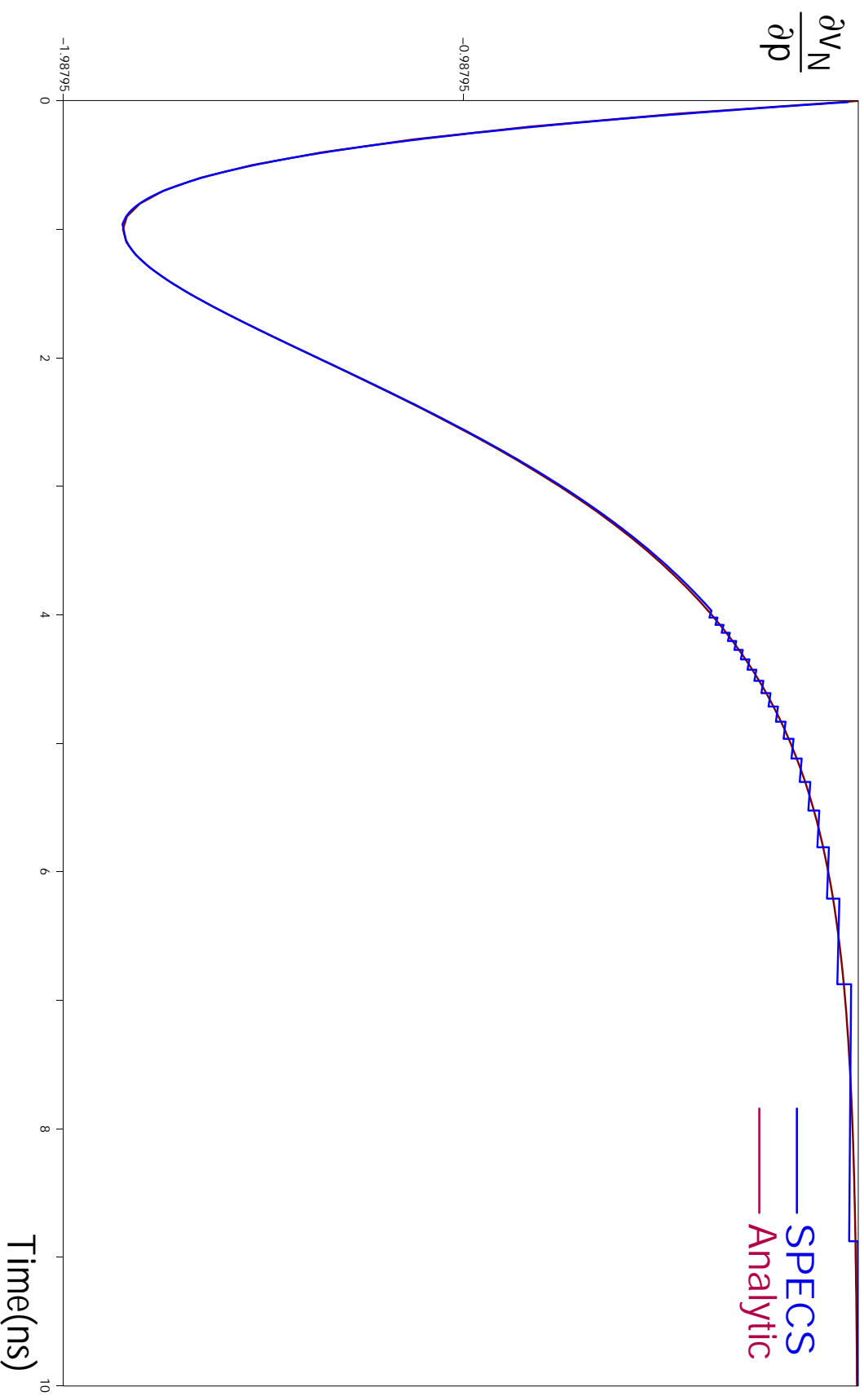

Part 4: Circuit Optimization

- designers spend OODLES of time manually tuning their (custom) circuits by adjusting transistor widths
- slow, tedious, error-prone process with circuit analysis in the inner loop

Given

- a circuit schematic with initial transistor sizes
- input signals or stimuli
- precise statement of circuit performance requirements


Determine

- optimal transistor size assignments

While supporting...

- flexible objective functions and constraints
- simple bounds
- ratio-ing of transistors and grouping of similar structures
- delay, rise/fall time, area and power measurements
- minimax optimization: $\text{Min } [\text{Max } \{ f_i(\underline{x}) \}]$
- easy-to-use graphical user interface in schematic environment

JiffyTune Overview

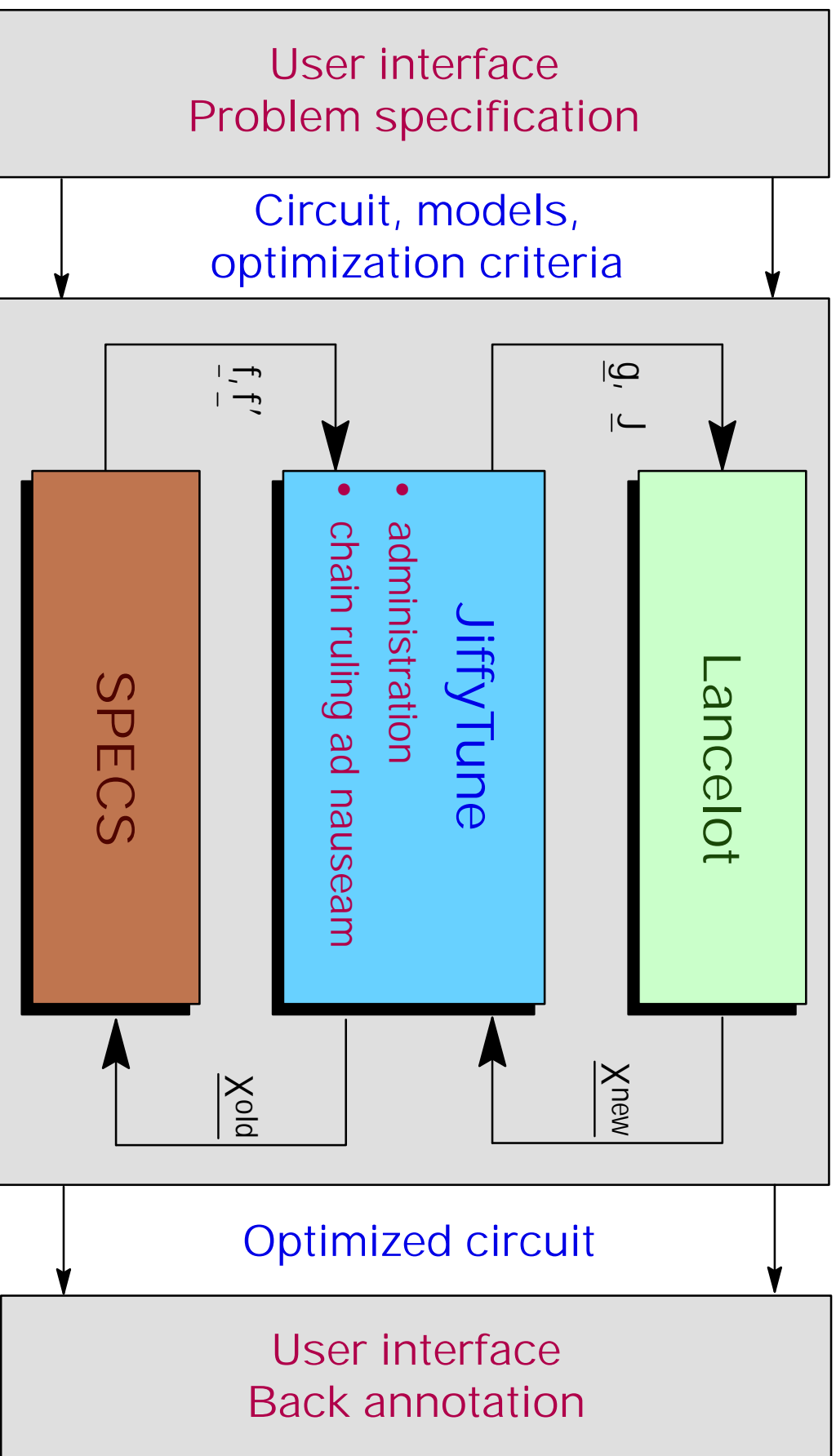

What is Lancelot?

- general-purpose nonlinear optimization package
- designed for large-scale problems for which it is remarkably robust
- efficient, especially for nonlinear constraints
- competitive for small and medium sized problems


Problem size and history

- has successfully handled 20,000 variable problems with 20,000 nonlinear constraints
- has been tested on 15,000 test cases representing 1,000 unique problems

Technical features

- augmented Lagrangian to handle general constraints
- simple bounds handled explicitly and well
- trust region approach
- many options available
 - l_∞/l_2 trust-region
 - approximate / accurate bounded quadratic problem (BQP) solver
 - various preconditioners, different initializations

How Lancelot Works

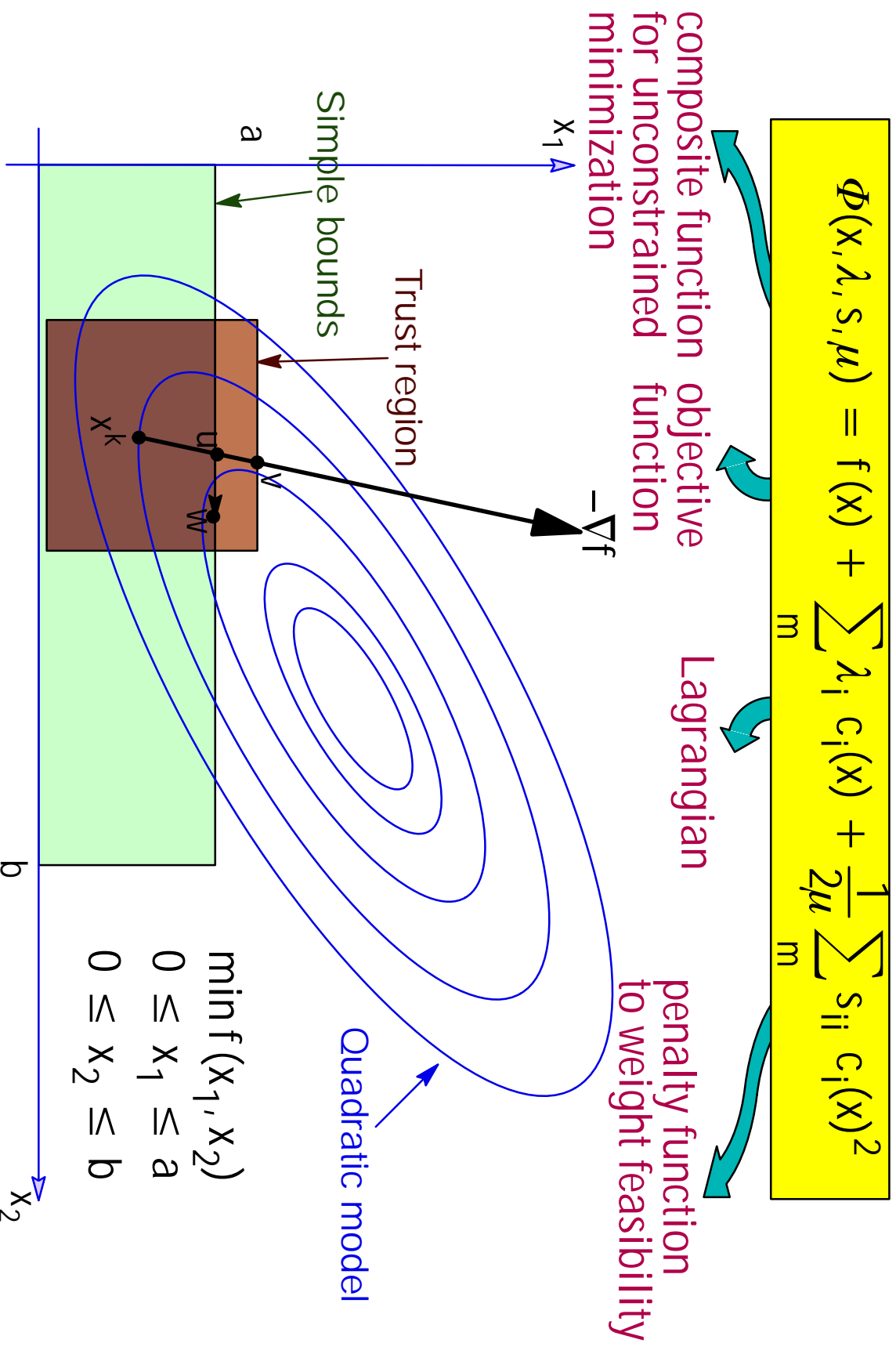

Minimax Optimization

Original problem

$$\text{Min}_{\underline{x}} [\text{Max}_i \{ f_i(\underline{x}) \}]$$

Remapped problem

$$\text{Min } (kz)$$

$$\text{Subject to } kz > f_i(\underline{x}) \quad \text{for all } i$$

Special considerations

- the scaling constant k helps create a well-scaled problem and helps with stopping criteria
- kz is initialized to the largest of the $f_i(\underline{x})$'s after the first function evaluation

Lancelot: Special Issues

Problems due to noise

- unable to recover from poor initializations
- optimizer wastes time going nowhere
- does not stop gracefully or predictably

Special considerations for noisy optimization

- tolerance for feasibility
- tolerance for line search break points
- consideration of small step beneath which further progress unlikely
- initial trust region radius
- initial Hessian approximation for secant methods
- stopping criteria

Miscellaneous

- slack variables updated at each major iteration
- testing environment has allowed us to integrate MINOS from Stanford as an alternative optimizer

Conclusions


Conclusions

1. By simplifying device models, we are able to perform fast, event-driven circuit analysis.
2. The simplified analysis lends itself to efficient time-domain gradient computation by both the direct and adjoint methods.
3. The simulation and gradient computation has been placed in the inner loop of a nonlinear optimization package to tune custom circuits.


Future work

1. Improve adjoint sensitivity performance by event-driven convolution; compute gradients in parallel.
2. Accommodate semi-infinite constraints; perhaps extend JiffyTune to solve manufacturability problems.
3. Automatic recovery from non-working circuits.
4. Investigate efficient computation of the Hessian.

SPECS

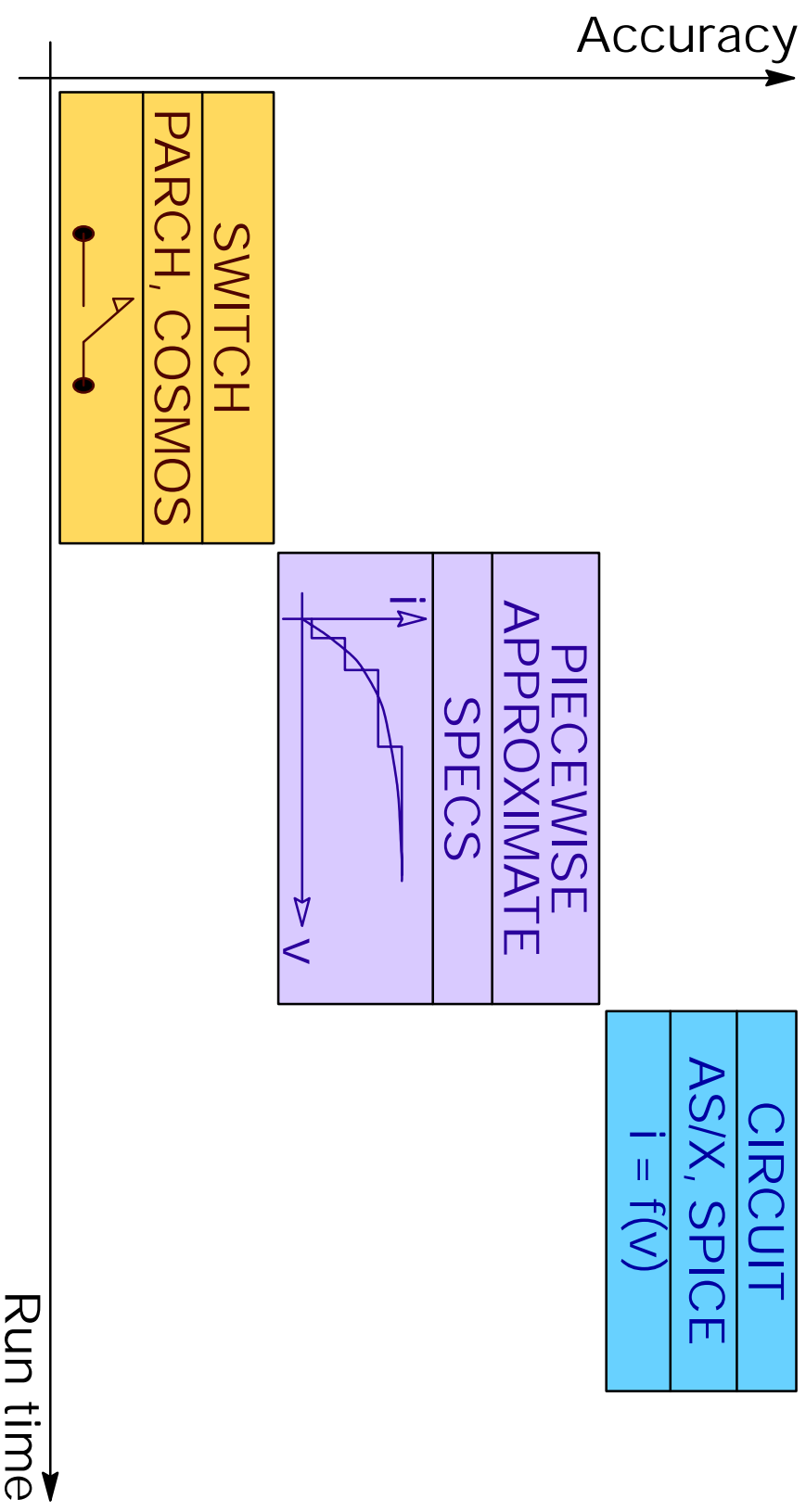

Static vs. Dynamic Tuning

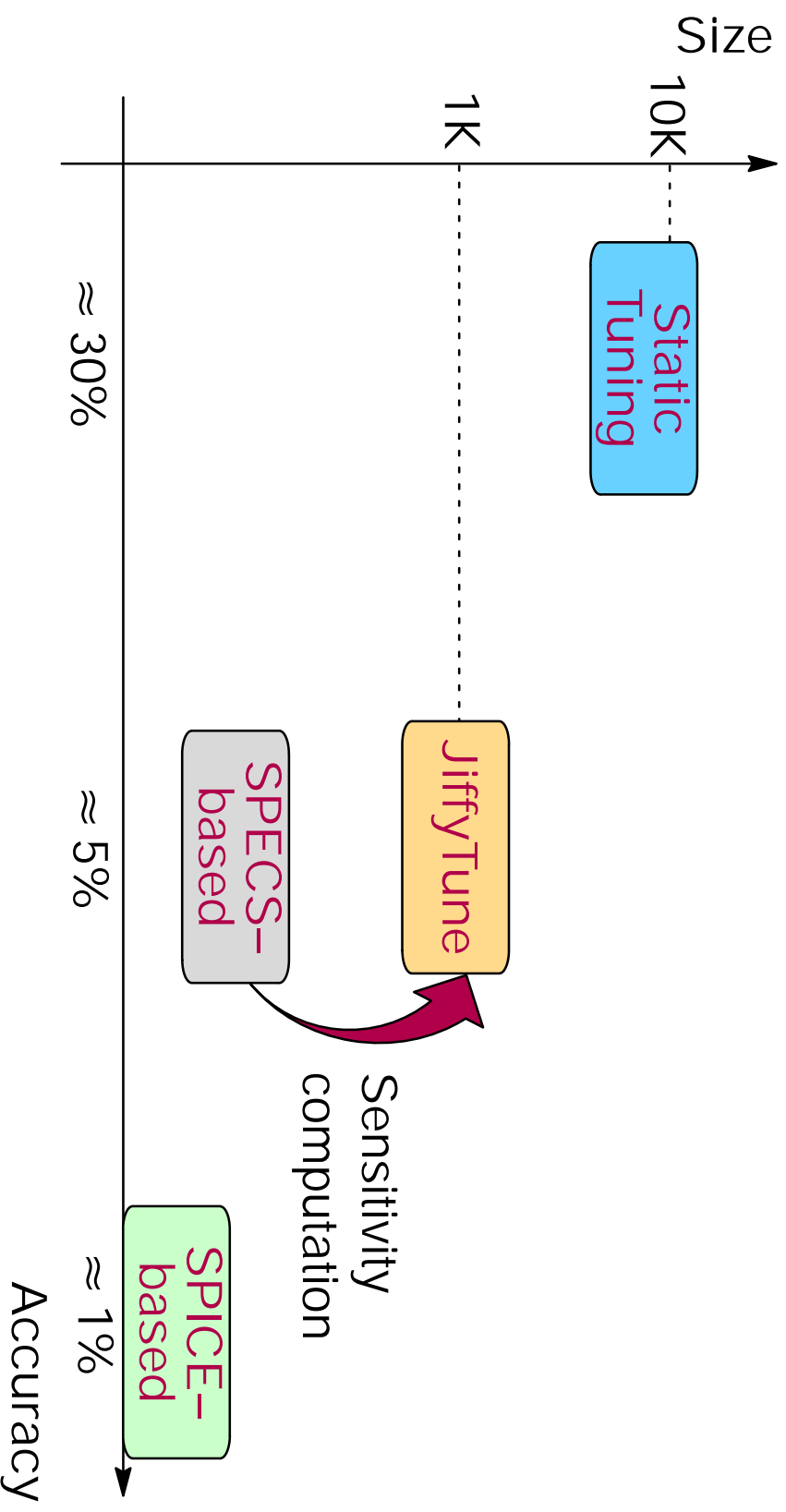

- need for pre-characterization
- applicability to custom circuits
- false-path problem vs. need for input vectors

Static and dynamic tuning complement each other!